

IPA Assignment-1

AND32:

We are given two 32-bit numbers a and b. We are expected to do bitwise AND operation and produce the output y.

Code:

```
`timescale 1ns / 1ps
`include "single.v"

module andgate(a,b,y);
input [31:0] a,b;
output [31:0] y;
genvar i;

    for(i=0; i<32; i=i+1)
    begin
        single temp (a[i], b[i], y[i]);
    end
endmodule
```

- In the code, we initially define our timescale to be 1ns/1ps. The time delays are measured in nanosecond and the precision is 1picosecond.
- We included single.v which contains a module which does AND operation between two bits.
- We defined genvar i; which is used to define the loop variable.
- We are asked to do the bitwise AND of 32 bits. So we run a for loop where we call the module single (it performs $a[i] \& b[i]$ to give $y[i]$).
- After running the loop, we finally get y in which each bit is the AND of a and b.

Test bench:

```
`timescale 1ns / 1ps

module andgate_test;

    //input
    reg [31:0]a;
    reg [31:0]b;

    //output
    wire [31:0]y;

    andgate uut (
        .a(a),
        .b(b),
        .y(y)
    );

    initial begin

        $dumpfile("andgate_test.vcd"); //used for dumping the waveform in a file that is opened by gkt
        $dumpvars(0,andgate_test); // used for dumping values in the file which we execute
        a = 32'b11111111111111111111111111111111;
        b = 32'b11111111111111111111111111111111;

        [

            // Add stimulus here
            #100 b=32'b011101110001111111111111100000001;
            #100 a=32'b000000111010111101010101010100;
            b=32'b00000000000000000000000000000000;
            #100 a=32'b11000001010111011111100000110001;
            b=32'b11111110011110111111010101010111;
            #100;

        ]

        initial begin
            $monitor("a=%b b=%b y=%b\n",a,b,y);
        end
    end


endmodule
```

- Writing the test which is responsible for testing the module that we have written is fairly simple.
- We define what the input and outputs are initially. Later, we instantiate the unit under test.
- Then we dump the waveforms into a file so that we can open that file in gtkwave later.
- We also use dumpvars to see that all the values of the instantiated variables are dumped into a file which we later use for executing.
- Then we actually give the values for a and b, then change them with appropriate delays. Later we print all of them in the monitor.


Terminal output:

```
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ iverilog -o andgate andgate_test.v andgate.v
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ vvp andgate
VCD info: dumpfile andgate_test.vcd opened for output.
a=11111111111111111111111111111111 b=11111111111111111111111111111111 y=11111111111111111111111111111111
a=11111111111111111111111111111111 b=0111011100011111111111000000001 y=0111011100011111111111000000001
a=000000111010111101010101010100 b=00000000000000000000000000000000 y=00000000000000000000000000000000
a=11000001010111011111100000110001 b=111111100111101111110101010111 y=11000000010110011111000000010001
```

GTKwave output:

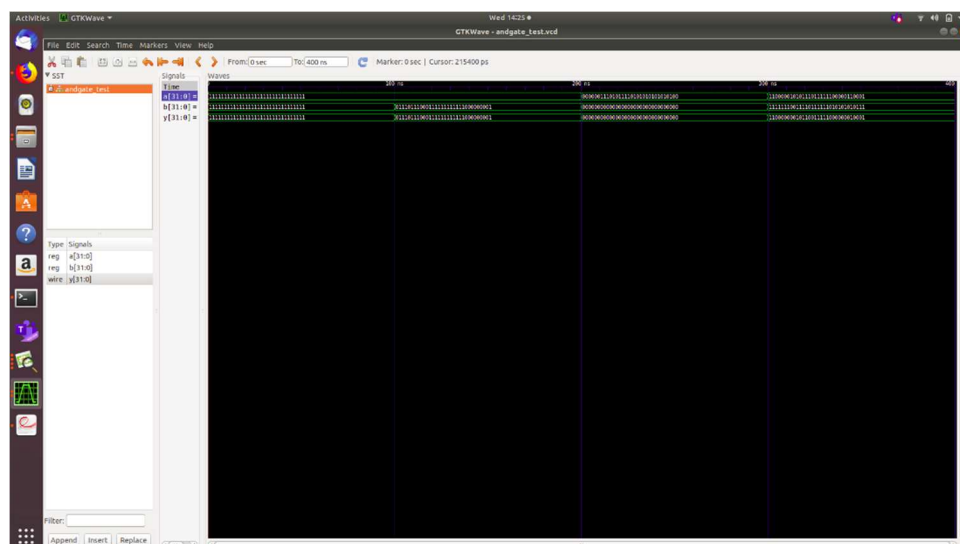

Due to lack of visibility in the above file, a pdf version saved is shown below.

 

XOR32:

We are given two 32-bit numbers a and b. We are expected to do bitwise XOR operation and produce the output y.

Code:

```
`timescale 1ns / 1ps
`include "single1.v"

module xorgate(a,b,y);
input [31:0] a,b;
output [31:0] y;
genvar i;

    for(i=0; i<32; i=i+1)
    begin
        single1 temp (a[i], b[i], y[i]);
    end
endmodule
```

- In the code, we initially define our timescale to be 1ns/1ps. The time delays are measured in nanosecond and the precision is up to 1picosecond.
- We included single1.v which contains a module which does XOR operation between two bits.
- We defined genvar i; which is used to define the loop variable.
- We are asked to do the bitwise XOR of 32 bits. So we run a for loop where we call the module single1(it performs $a[i] \oplus b[i]$ to give $y[i]$).
- After running the loop, we finally get y in which each bit is the XOR of a and b.

Test bench:

```
timescale 1ns / 1ps

module xorgate_test;

    //input
    reg [31:0]a;
    reg [31:0]b;

    //output
    wire [31:0]y;

    xorgate uut (
        .a(a),
        .b(b),
        .y(y)
    );

    initial begin
        $dumpfile("xorgate_test.vcd"); //used for dumping the waveform in a file that is opened by gkt
        $dumpvars(0,xorgate_test); // used for dumping values in the file which we execute
        a = 32'b11111111111111111111111111111111;
        b = 32'b11111111111111111111111111111111;

        #100 b=32'b011101110001111111111111100000001;
        #100 a=32'b000000011101011110101010101010100;
        b=32'b000000000000000000000000000000000;
        #100 a=32'b11000001010111011111100000110001;
        b=32'b111111100111101111111010101010111;
        #100;
    end

    initial begin
        $monitor("a=%b b=%b y=%b\n",a,b,y);
    end
endmodule
```


- Writing the tesbench which is responsible for testing the module that we have written is fairly simple.
- We define what the input and outputs are initially. Later, we instantiate the unit under test.
- Then we dump the waveforms into a file so that we can open that file in gtkwave later.
- We also use dumpvars to see that all the values of the instantiated variables are dumped into a file which we later use for executing.
- Then we actually give the values for a and b, then change them with appropriate delays. Later we print all of them in the monitor.

Results:



Terminal output:

```
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ iverilog -o xorgate xorgate_test.v xorgate.v
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ vvp xorgate
VCD info: dumpfile xorgate_test.vcd opened for output.
a=11111111111111111111111111111111 b=11111111111111111111111111111111 y=00000000000000000000000000000000
a=11111111111111111111111111111111 b=011101110001111111111111100000001 y=10001000111000000000000111111110
a=000000011101011110101010101010100 b=000000000000000000000000000000000 y=000000111010111101010101010100
a=11000001010111011111100000110001 b=11111110011110111111010101010111 y=00111111001001100000110101100110
```

GTKwave output:

 


Due to lack of visibility in the above file, a pdf version saved is shown below.

  

ADD32:

We are given two 32-bit signed numbers a and b . We are expected to add the numbers and produce the output y .

Theory behind the adder:

 

The above figure depicts a full adder. The basic idea is that when we add 3 bits, we get a sum and a carry bit.

We have two 32 bit numbers

$$\begin{array}{r} A_{31} A_{30} \dots A_2 A_1 A_0 \\ + \quad B_{31} B_{30} \dots B_2 B_1 B_0 \\ \hline \end{array}$$

- Now, initially, we have two bits A_0 , B_0 . Take $C_{in}=0$ ($C_0=0$). Then we get sum and carry. The sum represents Y_0 whereas the carry C_1 is taken as C_{in} for the second bit addition where we are expected to add A_1 , B_1 , C_1 . Now, we get the sum Y_1 and carry C_2 which is provided as C_{in} for the next operation.
- We repeat this for all the bits to get Y_{31} in the last step along with C_{32} . This process of building an adder sees carry out generated from carry in. So this gives the adder the name ripple carry adder.
- The last carry C_{32} is the 33rd bit. It gives us information about overflow. This is a very basic and intuitive method of solving the question. One might use carry look ahead and other methods for even more effective ways.

Code:

```
`timescale 1ns / 1ps
`include "operation.v"
`include "copy.v"

module adder(a, b, y1, y);
input [31:0] a, b;
output [31:0] y1;
output [32:0] y;
genvar i;
wire [32:0] carry;
assign carry[0]=0;

    for(i=0; i<32; i=i+1)
    begin
        operation temp (a[i], b[i], carry[i], carry[i+1], y1[i]);
    end

    for(i=0; i<32; i=i+1)
    begin
        copy temp (y1[i], y[i]);
    end
assign y[32]=carry[32];
endmodule
```

- We have defined the timescale and include the necessary modules. Here, the adder module contains inputs a and b. The outputs are y1 and y. We need two outputs due to the fact that there might be an overflow resulting in a 33rd bit.
- Y1 is the output corresponding to the 32 bit answer whereas y corresponds to the actual 33 bit output possible. The first bit(most significant bit) in y indicates an overflow by showing 1 and it shows 0 when there is no overflow.
- The carry array is of 33 bit length and we take the initial carry bit carry[0]=0. Now, we pass the parameters a[i], b[i], carry[i] as inputs in a module operation where we get outputs carry[i+1] and y1[i];
- In operation module we take
- **$y1[i] = a[i] \oplus b[i] \oplus c[i]$**
- **$carry[i+1] = ((a[i] \oplus b[i]) \& carry[i]) \vee a[i] \& b[i]$**
- Now, we get y1[i] which is the 32bit answer neglecting the last carry bit.
- To include that bit as well, we write a loop where we assign y[i]=y1[i] and take the last bit y[32]=carry[32].

Test bench:

```
timescale 1ns / 1ps

module adder_test;

    // Inputs
    reg [31:0]a;
    reg [31:0]b;

    // Outputs
    wire [31:0]y1;
    wire [32:0]y;

    // Instantiate the Unit Under Test (UUT)
    adder uut (
        .a(a),
        .b(b),
        .y1(y1),
        .y(y)
    );
    initial begin
        $dumpfile("adder_test.vcd");
        $dumpvars(0,adder_test);

        a = 32'b01001111000001001001000110000001;
        b = 32'b01000000011100001100010001110001;

        #100; a = 32'b0000000000000000000000000000010;
        b = 32'b11111111111111111111111111111111;

    end
    initial begin
        $monitor("a=%b b=%b 32bity=%b 33bity=%b \n",a,b,y1, y);
    end
endmodule
```

Writing the test bench is similar to that of the previous cases. There is nothing new done for adder.

Results:

Terminal output:

```
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ iverilog -o adder adder_test.v adder.v
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ vvp adder
VCD info: dumpfile adder_test.vcd opened for output.
a=001011110000010010001100000001 b=01000000011100001100010001110001 32bity=01101111011101010101010111110010 33bity=00110111110111010101010111110010
a=10000000000000000000000001100010 b=0011001111111100011011110000011 32bity=1011001111111100011011111100101 33bity=010110011111111100011011111100101
a=00000000000000000000000000000001 b=11111111111111111111111111111111 32bity=00000000000000000000000000000001 33bity=10000000000000000000000000000001
a=1010101111110101010101010101111 b=100000000111111111110000000000 32bity=00101100001101001010011010101111 33bity=100101100001101001010011010101111
```

Time		100 ns
a[31:0]	00101111000001001001000110000001	100000000000000000000000000000001100010
b[31:0]	01000000011100001100010001110001	00110011111111100011011110000011
y1[31:0]	011011110111010101010111110010	10110011111111100011011111100101
y[32:0]	0011011110111010101010111110010	01011001111111100011011111100101

[illegible]

Subtract32:

We are given two 32-bit signed numbers a and b . We are expected to subtract b from a (i.e. $a-b$) and produce the output y .

Theory behind the subtractor:

- We are expected to implement a subtractor. $a-b=a+(-b)$. So now, if we are able to find out the value of $-b$, we can add a and $-b$ to get the output.
- We know that to find $-b$, the method is by taking 2's complement.
- To find 2's complement of a number b , we just have to flip the bits of it. This means that for each of the 32 bits, if we have 1, we make it 0 and if we have 0, we make it 1.
- Now to this flipped number say $\sim b$, we need to add 1. This means that we pass $\sim b$, 1 as input to the adder and get $-b$.
- Now, since we have a , $-b$ we pass them in the adder to get $y1$ (32 bit answer) and y (33 bit answer). The extra bit is to accommodate an overflow incase any.

Code:

```
`include "negate.v"
`include "adder.v"
module subtractor(a, b, y1, y);
input[31:0] a, b;
output [31:0] y1;
output [32:0] y;

wire[31:0] bcomp;
wire[31:0] b2comp;
genvar i;
for(i=0; i<32; i=i+1)
begin
    negate temp(b[i],bcomp[i]);
end

assign number=32'b1;
adder temp (bcomp, number, b2comp, waste);
adder temp1 (a, b2comp, y1, y);
endmodule
```

- We include the necessary modules in the beginning and then define the inputs and outputs. We define temporary arrays, bcomp and b2comp.
- We write a for loop that takes b[i] as input and returns the output as $\sim b[i]$.
- All these values are stored in the vector bcomp. Then we pass bcomp and 1 into the adder(which adds the two numbers) to get b2comp.
- Now, we simply pass a and b2comp into the adder to get y1(32 bit) output and y(33 bit output).

Test bench:

```
timescale 1ns / 1ps

module subtractor_test;

    // Inputs
    reg [31:0]a;
    reg [31:0]b;

    // Outputs
    wire [31:0]y1;
    wire [32:0]y;
    // Instantiate the Unit Under Test (UUT)
    subtractor uut (
        .a(a),
        .b(b),
        .y1(y1),
        .y(y)
    );

    initial begin
        $dumpfile("subtractor_test.vcd");
        $dumpvars(0,subtractor_test);

        a = 32'b00101111000001001001000110000001;
        b = 32'b0100000001110000110001000110001;

        #100; a = 32'b10000000000000000000000001100010;
        b = 32'b001100111111111100011011110000011;

        #100; a = 32'b0000000000000000000000000000010;
        b = 32'b11111111111111111111111111111111;

        #100; a = 32'b10101011111101001010101010101111;
        b = 32'b100000000011111111111111100000000;

    end

    initial begin
        $monitor("a=%b b=%b 32bit=%b 33bit=%b\n",a,b,y1, y);
    end

endmodule
```

The test bench follows the same procedure. Just defining the inputs, outputs, instantiating, dumping in necessary files and displaying input and output on monitor.


Results:

Terminal output:

```
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ vln subtractor.v
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ vln subtractor_test.v
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ iverilog -o subtractor subtractor_test.v subtractor.v
subtractor.v:17: warning: Port 2 (b) of adder expects 32 bits, got 1.
subtractor.v:17:      : Padding 31 high bits of the port.
subtractor.v:17: warning: Port 4 (y) of adder expects 33 bits, got 1.
subtractor.v:17:      : Padding 32 high bits of the port.
surya@surya-HP-Laptop-15-da0xxx:~/sem4/ipa1/IPA_tutorial/alu$ vvp subtractor
VCD info: dumpfile subtractor_test.vcd opened for output.
a=00101111000001001001000110000001 b=0100000001110000110001000110001 32bit=11101110100100111100110100010000 33bit=011101110100100111100110100010000
a=10000000000000000000000001100010 b=0011001111111100011011110000011 32bit=01001100000000011100100011011111 33bit=10100110000000011100100011011111
a=000000000000000000000000000000010 b=11111111111111111111111111111111 32bit=000000000000000000000000000011 33bit=0000000000000000000000000000011
a=101010111110100101010101011111 b=10000000001111111111000000000 32bit=0010101110110100101011010101111 33bit=10010101110100101011010101111
```

Note that the warnings are due to the fact that we are adding 32b'1(which is representation of 1). So the remaining bits are 0 padded which is expected already.

GTKwave output:

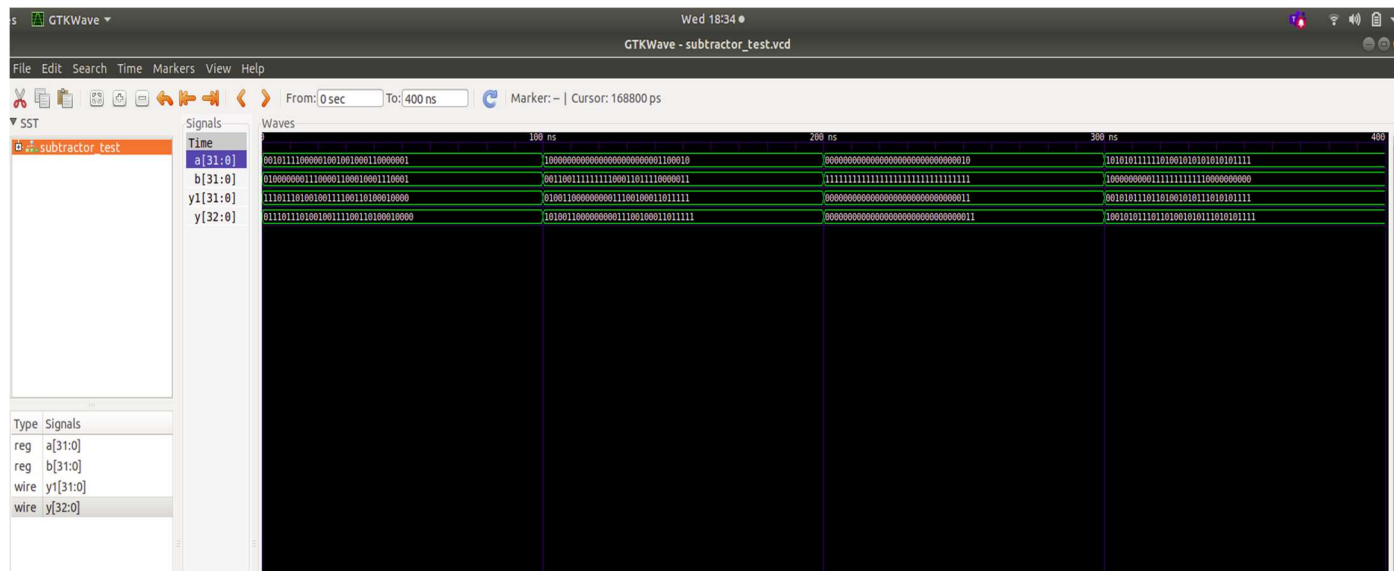

Due to lack of visibility in the above file, a pdf version saved is shown below.

Time		100 ns
a[31:0]	00101111000001001001000110000001	100000000000000000000000000000010
b[31:0]	01000000011100001100010001110001	0011001111111100011011110000011
y1[31:0]	1110111010010011100110100010000	01001100000000011100100011011111
y[32:0]	011101110100100111100110100010000	101001100000000011100100011011111

	200 ns	300 ns	400 ns
	000000000000000000000000000000010	10101011111101001010101010101111	
	111111111111111111111111111111111	1000000001111111111100000000000	
	000000000000000000000000000000011	0010101110101001010111010101111	
	000000000000000000000000000000011	100101011101101001010111010101111	

ALU32:

Now, our final goal is to combine the all the above question using a select line

c. If, c=0 perform AND between a and b

c=1 perform XOR between a and b

c=2 perform addition between a and b

C=3 perform subtraction between a and b

Code:

```
`timescale 1ns / 1ps
`include "andgate.v"
`include "xorgate.v"
`include "subtractor.v"

module alu(a, b, c, y);
input [31:0] a, b;
input [1:0] c;
output reg [31:0] y;

reg[31:0] con;
wire[31:0] y0;
wire[31:0] y1;
wire[31:0] y2;
wire[31:0] y3;

andgate temp2(a, b, y0);
xorgate temp3(a, b, y1);
adder temp0 (a, b, y2, waste);
subtractor temp1(a, b, y3, junk);

always @ (*)
case(c)
0: y<=y0;
1: y<=y1;
2: y<=y2;
3: y<=y3;
endcase
```

The code is self explanatory. We include the necessary modules. We mention what the inputs and outputs are. Then we take 4 wires which are used to store the computed values of the operations from 0 to 4. Then we write a case statement where depending upon the value of c, we assign y to one of yi.

Test bench:

Writing the test bench is slightly longer here. The overall procedure is the same but the values which we take and want to check make the testbench long. The values which we take are

```
a = 32'b00101111000001001001000110000001;
b = 32'b01000000011100001100010001110001;
c=00;

#100; a = 32'b10000000000000000000000001100010;
b = 32'b00110011111111100011011110000011;

#100; a = 32'b0000000000000000000000000000010;
b = 32'b11111111111111111111111111111111;

#100; a = 32'b10101011111101001010101010101111;
b = 32'b1000000000111111111110000000000;
#100;

a = 32'b00101111000001001001000110000001;
b = 32'b01000000011100001100010001110001;
c=01;

#100; a = 32'b10000000000000000000000001100010;
b = 32'b00110011111111100011011110000011;

#100; a = 32'b0000000000000000000000000000010;
b = 32'b11111111111111111111111111111111;

#100; a = 32'b10101011111101001010101010101111;
b = 32'b1000000000111111111110000000000;
#100;
a = 32'b00101111000001001001000110000001;
b = 32'b01000000011100001100010001110001;
c=10;

#100; a = 32'b10000000000000000000000001100010;
b = 32'b00110011111111100011011110000011;

#100; a = 32'b0000000000000000000000000000010;
b = 32'b11111111111111111111111111111111;

#100; a = 32'b10101011111101001010101010101111;
b = 32'b1000000000111111111110000000000;
#100;
```



```
a = 32'b001011111000001001001000110000001;
b = 32'b01000000011100001100010001110001;
c=11;

#100; a = 32'b10000000000000000000000001100010;
b = 32'b00110011111111100011011110000011;

#100; a = 32'b0000000000000000000000000000010;
b = 32'b11111111111111111111111111111111;


#100; a = 32'b10101011111101001010101010101111;
b = 32'b10000000001111111111110000000000;
#100;
```

Results:

Terminal output:

```
VCD info: dumpfile alu_test.vcd opened for output.
a=00101111000001001001000110000001 b=01000000011100001100010001110001 y=0000000000000000100000000000001 c=00
a=10000000000000000000000001100010 b=0011001111111100011011110000011 y=00000000000000000000000000010 c=00
a=0000000000000000000000000000010 b=11111111111111111111111111111111 y=00000000000000000000000000010 c=00
a=10101011111101001010101010101111 b=10000000001111111111000000000 y=100000000110100101010000000000 c=00
a=00101111000001001001000110000001 b=01000000011100001100010001110001 y=01101111011101000101010111110000 c=01
a=10000000000000000000000001100010 b=0011001111111100011011110000011 y=101100111111110001101111110001 c=01
a=0000000000000000000000000000010 b=11111111111111111111111111111111 y=11111111111111111111111111101 c=01
a=10101011111101001010101010101111 b=10000000001111111111000000000 y=0010101111001011010101010101111 c=01
a=00101111000001001001000110000001 b=01000000011100001100010001110001 y=01101111011101010101010111110010 c=10
a=10000000000000000000000001100010 b=0011001111111100011011110000011 y=1011001111111100011011111100101 c=10
a=0000000000000000000000000000010 b=11111111111111111111111111111111 y=0000000000000000000000000001 c=10
a=10101011111101001010101010101111 b=10000000001111111111000000000 y=00101100001101001010011010101111 c=10
a=00101111000001001001000110000001 b=01000000011100001100010001110001 y=11101110100100111100110100010000 c=11
a=10000000000000000000000001100010 b=0011001111111100011011110000011 y=0100110000000011100100011011111 c=11
a=0000000000000000000000000000010 b=11111111111111111111111111111111 y=00000000000000000000000000011 c=11
a=10101011111101001010101010101111 b=10000000001111111111000000000 y=001010111101001010111010101111 c=11
```


GKTwave output:

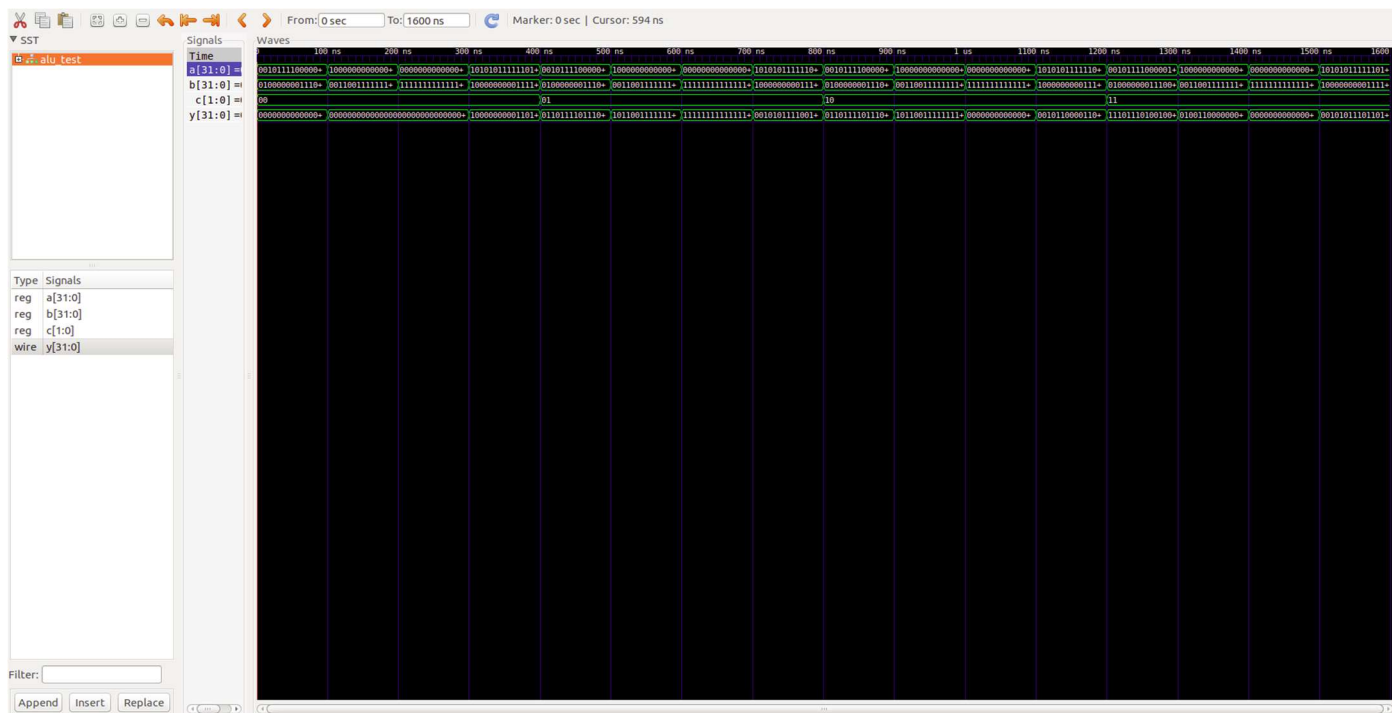

If we make a pdf, we need to attach a lot pictures. Since already the output of the terminal is attached above, zoomed plots are not added.

The following link contains all the plots and codes:

https://iiitaphyd-my.sharepoint.com/:f:/g/personal/sri_surya_students_iiit_ac_in/Elt-NZT5zhVCsKfWZ0tI3RABQym-O9W_0YpAMarUcFKzyQ?e=qJNlzw